

**ANSWER ALL QUESTIONS**

**Question One: (20 MARKS)**

1) Determine and draw  $V_o$  for the circuits of Fig.1

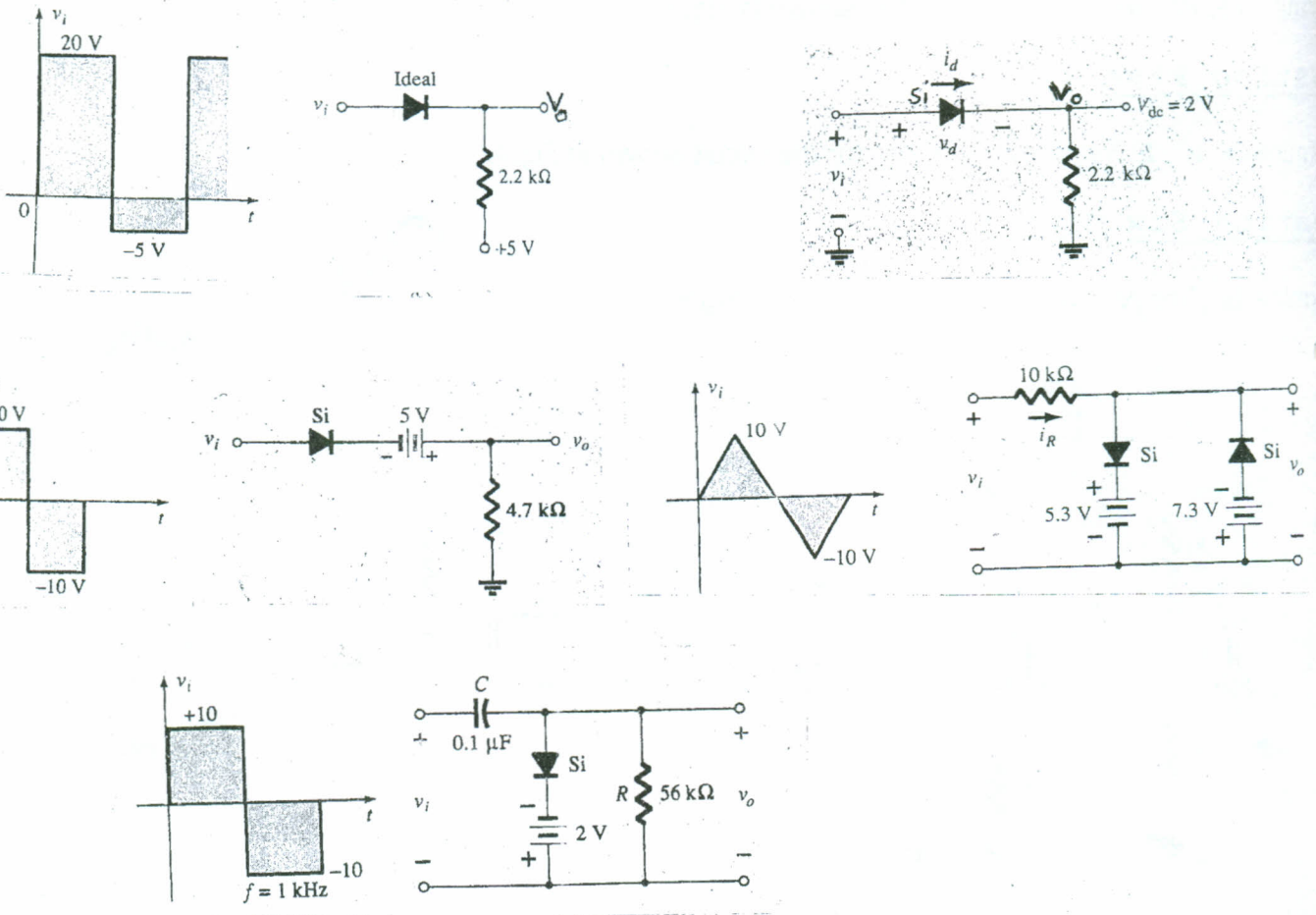


Fig.1

**Question Two: (10 MARKS)**

Determine the range of values of  $V_i$  that will maintain the Zener diode of Fig.1 in the ON- state

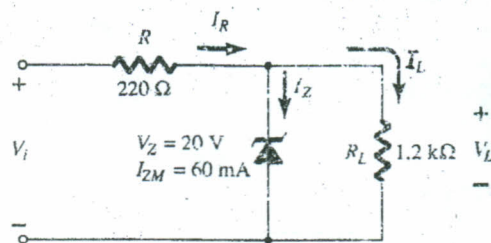


Fig.2

**Question Three:** ( 20 MARKS)

- a) What is the benefit of high input impedance in FET ? (3)
- b) Draw and discuss the output characteristics of BJT common emitter configuration. (5)
- c) Draw and explain the structure and operation of n-channel enhancement MOSFET and its output characteristics. (8)
- d) Prove that  $I_E = (1 + \beta) I_B$  &  $\alpha = \beta / 1 + \beta$  (4)

**Question Four:** (16)

Determine  $R_E, R_C, R_1, R_2$ , for the circuit shown in Fig.3.

**Question Five:** (18)

Determine  $I_B, I_C, I_E, V_B, V_C, V_E, V_{CB}, V_{CE}$  for the circuit shown in Fig.4.

**Question Six:** (16)

Determine  $I_D, V_{DS}, V_D, V_S$  for the circuit shown in Fig.5

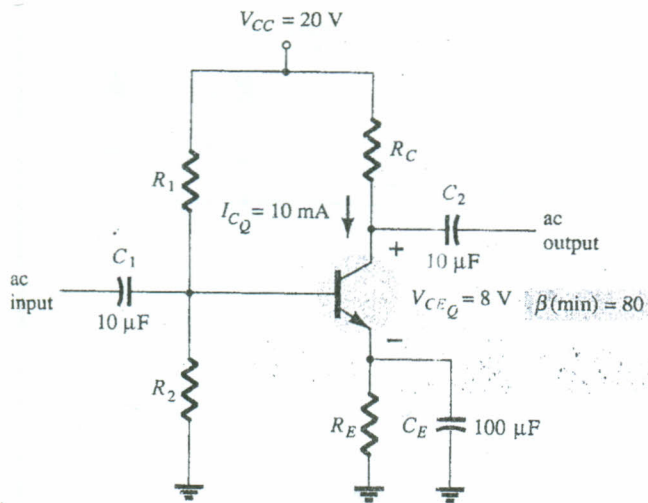


Fig.2

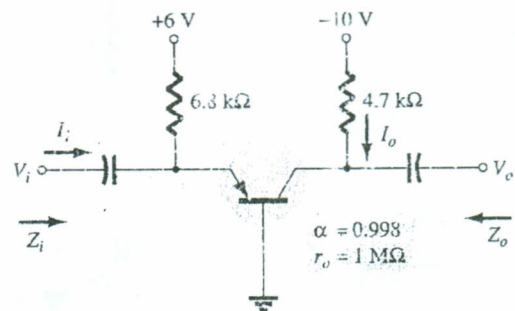


Fig.3

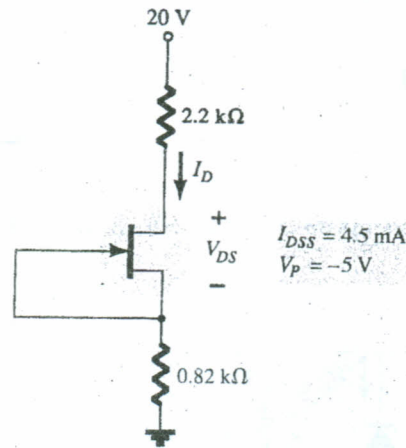


Fig.4

**Good Luck**