

”اختبار الآلات الكهربائية (الجزء الاول) نهاية الترم 2013 لتخصص اتصالات“

ANSWER ALL THE FOLLOWING QUESTIONS:

السؤال الأول :

- (أ) أذكر في خطوات كيف يمكنك توصيل مولدان على التوازي .وضح اجابتك بالرسم .
(ب) مولدان توازي وصلا على التوازي لتغذية حمل مقداره 800 أمبير . فاذا كانت مقاومة المنتج والمجال لكل منهما هي 0.05Ω ، 50Ω على الترتيب . وكانت قيمة القوة الدافعة الكهربائية لكل منهما هي $E_1 = 200 \text{ V}$ ، $E_2 = 210 \text{ V}$ على الترتيب . أوجد :
(i) عند أى جهد يتم تغذية الحمل .
(ii) القدره التي يغذيها كل مولد للحمل .

السؤال الثانى:

- (أ) استنتج جميع المعادلات اللازمة لحساب أجزاء مقاطع مقاومة بدء الحركة لمحرك توازي .
(ب) احسب كفاءة محرك مركب مستو طويل الذى قدرته 13.405 حصان، 200 فولت ، مقاومة لفات التوازي 100 أوم ، مقاومة لفات التوالى والمنتج هي 0.1 ، 0.4 أوم على الترتيب ، المفاقد الشاردة 520 واط ، هبوط تلامس الفرش عند الحمل الكامل 2 فولت . ثم ارسم منحنى الكفاءة مع تيار المنتج ، عندما تكون قيم تيارات المنتج 52 ، 42 ، 32 ، 22 أمبير . كذلك أوجد الكفاءة العظمى .

السؤال الثالث:

- (أ) إرسم واشرح بايجاز كيف يمكنك تعيين قيم المقاومات والممانعات للدائرة المكافئة التقريبية معمليا .
(ب) محول مقننه 230/ 2300 فولت ، 15 كيلو فولت أمبير ، 50 هيرتز ، $P_{e+h} = 92 \text{ watt}$.
 $N_1 = 1500 \text{ turn}$, $N_2 = 150 \text{ turn}$, $r_1 = 2.7 \Omega$, $x_1 = 9.1 \Omega$, $r_2 = 0.024 \Omega$, $x_2 = 0.088 \Omega$, $I_n = 0.15 \text{ A}$.
على فرض أن المحول يعمل عند معامل قدرة 0.8 متقدم ، وعند 10 كيلو فولت أمبير ، وعندما كان الجهد الطرفى لملفه الثانوى 230 فولت . احسب وارسم :
(i) الدائرة المكافئة التقريبية منسوبة لدائرة الملف الابتدائى مدونا عليها جميع قيم المقاومات والممانعات
(ii) ارسم مخطط المتجهات بمقياس رسم 1 : 200 فولت .
(iii) أوجد قيمة تنظيم الجهد والكفاءة .
(vi) أوجد الكفاءة العظمى عند معامل قدرة الوحدة .

" انظر ورقة اسئلة الجزء الثانى "



Final-term exam of (Electrical Machines)

For 2nd Grad Communications and electronics Engineering Dept. students.

Answer All Questions. الامتحان من جزأين: من فضلك أجب كل جزء من الامتحان في اتجاه مختلف من ورقة الإجابة.

First Question: (5 + 5 marks)

- Define the winding factor, show how it can be estimated, and explain why short-pitch windings is preferred over full-pitch windings?
- Draw the phasor diagram of synchronous generator at various load power factors and obtain a general formula that describes its E.M.F.

Second Question: (15 marks)

A 6.6 KV, three-phase, 10-pole, 50 Hz, star-connected synchronous alternator has 3 slots/pole/phase, 6 conductors/slot placed in two layers, and coil span of 140° elec.degree. The alternator gave the following test data:


Field current, A	32	50	75	100	140
O.C phase voltage, KV	1.79	2.83	3.81	4.33	4.79

A field current of 32A is found to cause rated current of 500A to flow through the armature windings during short-circuit test.

Armature resistance per-phase is 0.2 Ω. Calculate the voltage regulation and the corresponding per-pole flux at full-load, 0.8 leading p.f. using:

- E.M.F method
- M.M.F method

من فضلك، ارفق رسم لورقة الإجابة

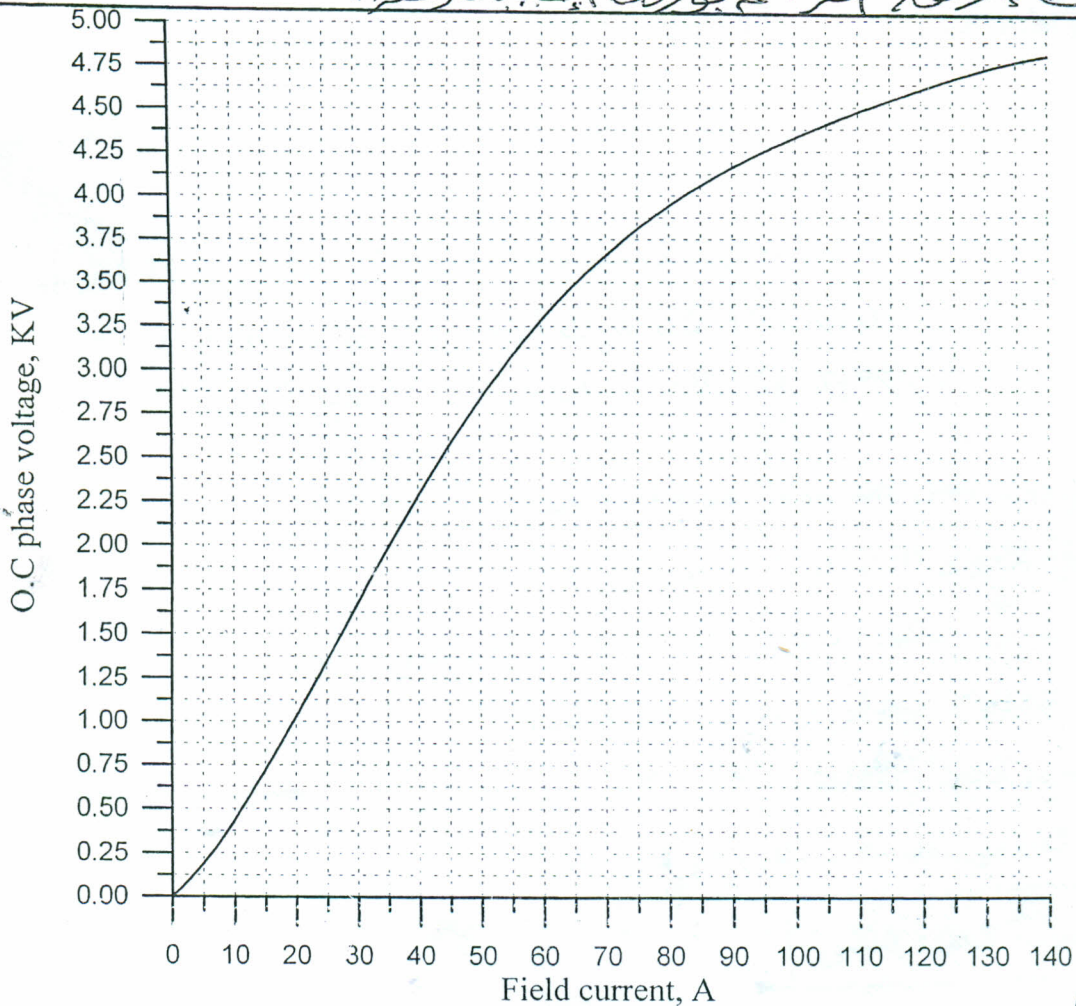

Third Question : (7 + 8 + 7 + 8 marks)

- 3-1) Deduce** the exact equivalent circuit of three-phase induction motor, then **Draw** the phasor diagram, and hence **deduce** the approximate equivalent circuit. **Explain** the experimental tests used to estimate the parameters of the exact equivalent circuit.
- 3-2) Explain** the methods adopted for starting the following motors:
- 3-phase induction motors with squirrel cage and slip-ring wound rotor types; and
 - Single phase induction motor with explaining why it has not starting torque?
- 3-3) State** the condition under which a three-phase induction machine will have:
- Rotor frequency equal to stator frequency,
 - Rotor speed higher than rotating field speed,
 - Maximum voltage and current induced in the rotor, and
 - Minimum voltage and current induced in the rotor.
- 3-4)** A three-phase, 4-pole, 50 Hz, induction motor running at full-load torque of 73.3 N.m. with speed of 1433 r.p.m. The friction and windage losses are 250 W, stator copper and iron losses amount 900 W. **Calculate:**
- Mechanical power,
 - Rotor copper loss, and
 - Efficiency.

Good Luck.

Prof. Dr. Mohamed El-Shamoty

Page 2 of 2